

Q2) For a given Boolean function **F** which has “don’t care” conditions as

$$\mathbf{F(A,B,C,D) = \Sigma m (3,6,8,11,12,13,14,15) + \Sigma d (0,1,5,7)}$$

- (a) Optimize **F** in the sum-of-products (SOP) form. Calculate Gate Input (G) cost.
- (b) Implement **F** with NAND gates only.
- (c) Optimize **F** in the product-of-sums (POS) form. Calculate Gate Input (G) cost.
- (d) Implement **F** with NOR gates only.