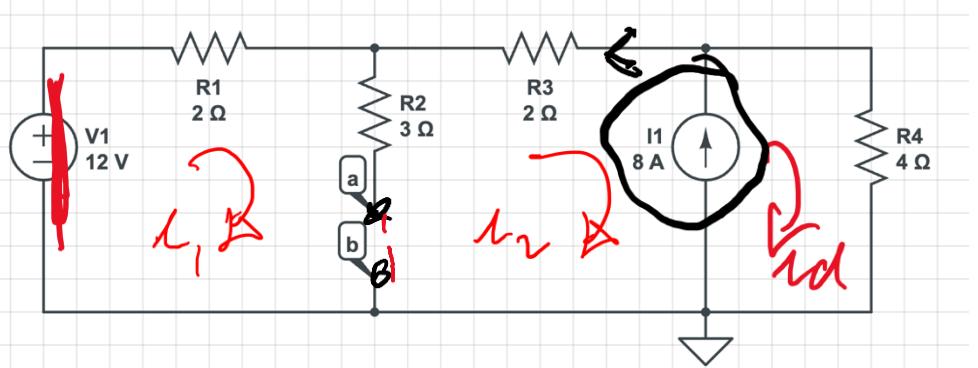


Review questions


Example 1



$$\frac{34}{9} \text{ A} \quad \left\{ \frac{9}{2} \right.$$

Norton's

Current source

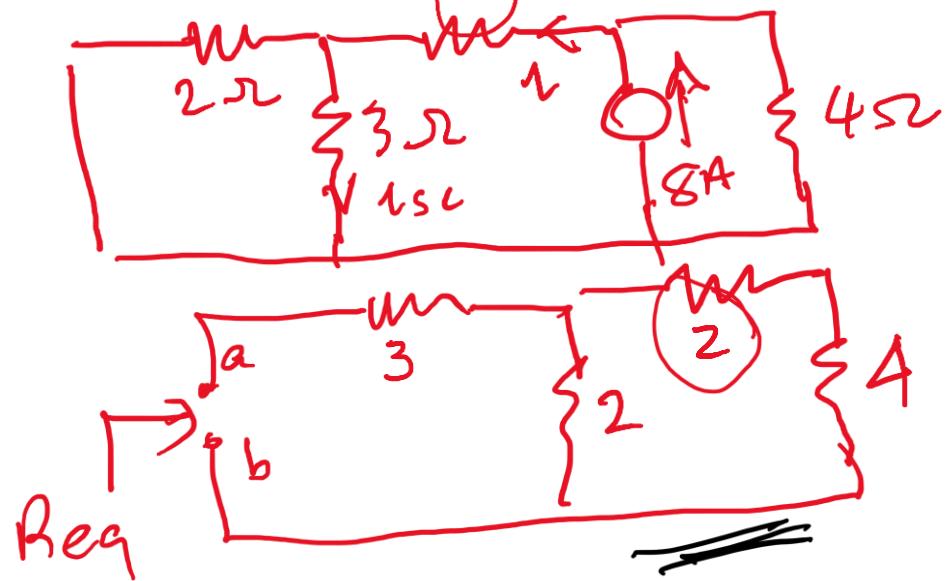

$$Req = \frac{9}{2}$$

for the voltage source


$$5I_1 - 3I_2 = 12$$

$$-3I_1 + 9I_2 = 0$$

Solve for I_1 and I_2

$$I_1 = 3 \text{ A} \quad I_2 = 1 \text{ A}$$

$$I_{SC} = 2 \text{ A}$$

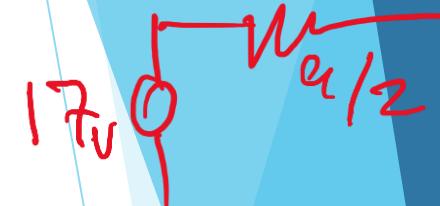

Thevenin's

2||(3+2) resistance on the left

$$\frac{6}{5} + 2 = \frac{16}{5}$$

$$i = \frac{8}{\frac{1}{4} + \frac{5}{16}} \cdot \frac{5}{16}$$


$$I_{SC_T} = 2 + \frac{16}{9} = \frac{34}{9}$$

$$I_{SC2} = \frac{\frac{40}{9}}{\frac{1}{2} + \frac{1}{3}} \cdot \frac{1}{3}$$

for the current source

Example 2

Find e_a / e_b using node voltages!

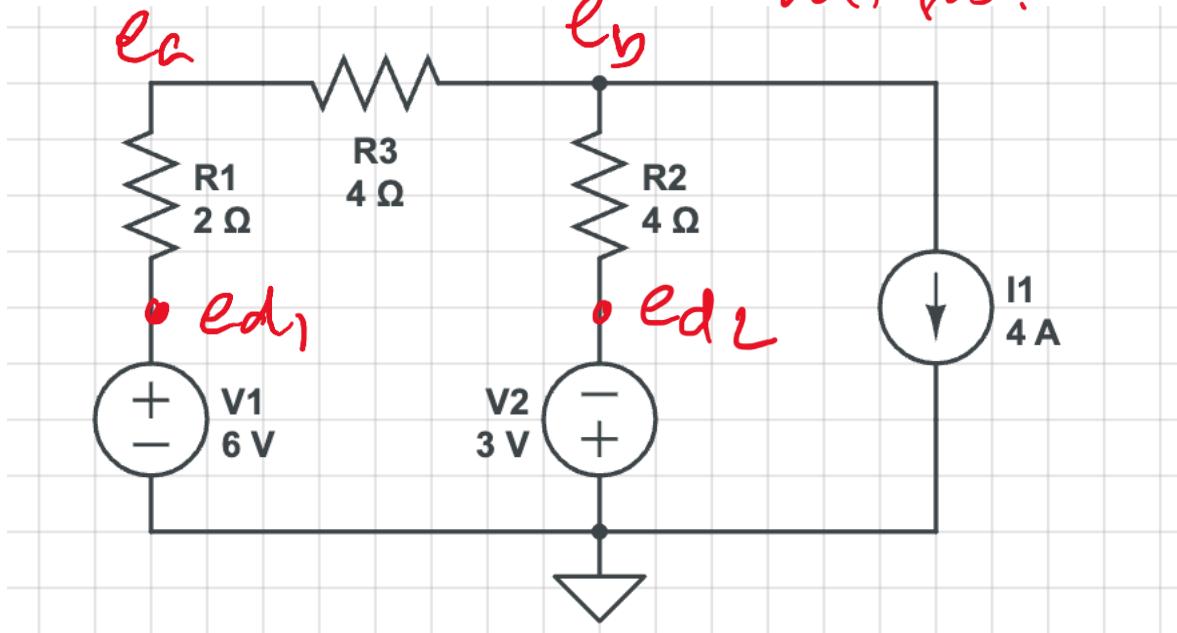


$$e_a \left(\frac{1}{2} + \frac{1}{4} \right) = \frac{e_b}{4} - \frac{e_{d1}}{2} = 0$$

$$- \frac{e_a}{4} + e_b \left(\frac{1}{4} + \frac{1}{4} \right) - \frac{e_{d2}}{4} = -4$$

$$e_{d1} = 6 \quad e_{d2} = -3$$

$$e_a = 1V \quad e_b = -9V$$

Example 3

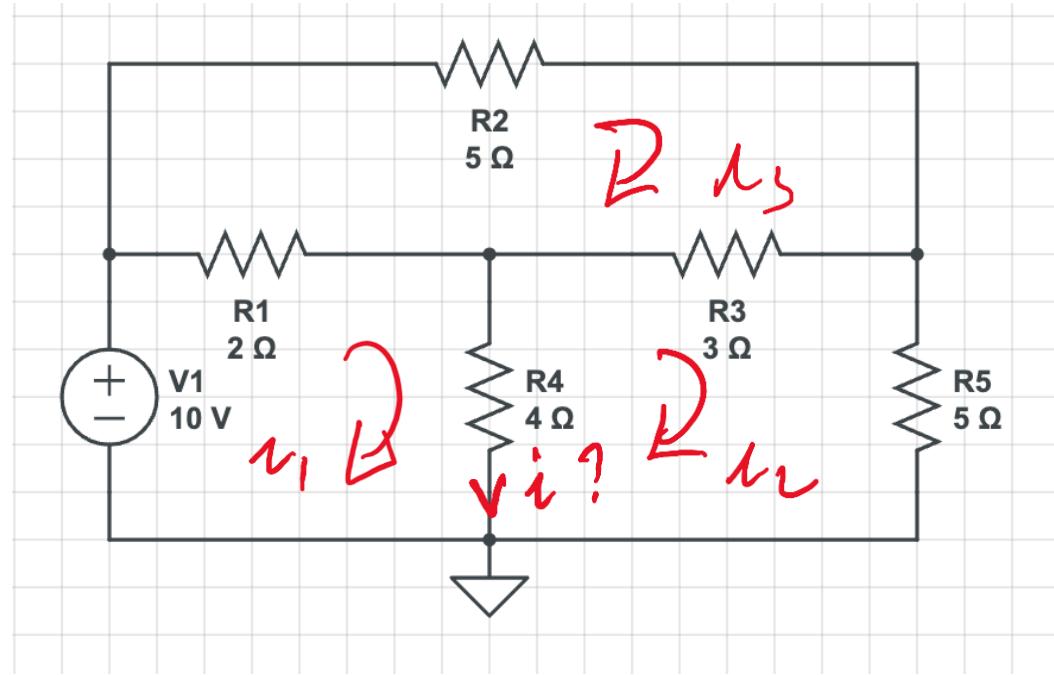


$$I_1 = 2 \cdot 71$$

$$I_2 = 1.12$$

$$I_3 = 0.87$$

$$I = I_1 - I_2 \\ = 1.58 \text{ A}$$

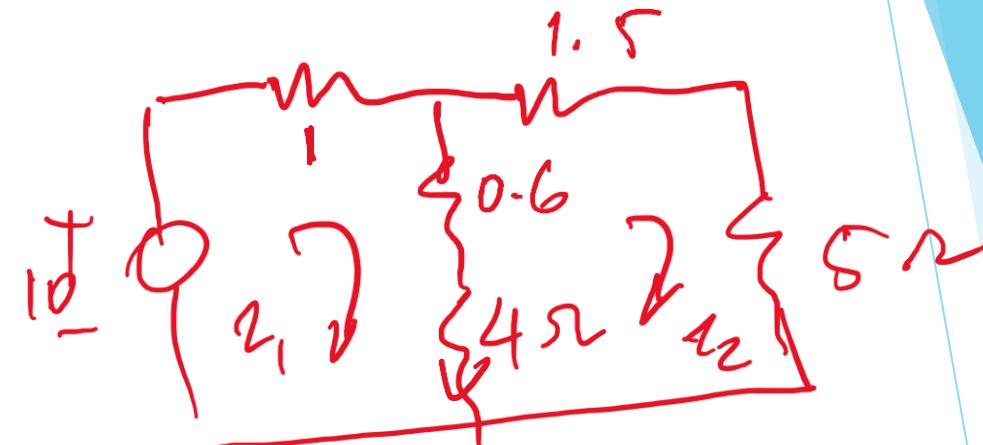


$$5.6I_1 - 4.6I_2 = 10$$

$$-4.6I_1 + 11.1I_2 = 0$$

$$I_1 = 2.7$$

$$I_2 = 1.12$$

Example 4

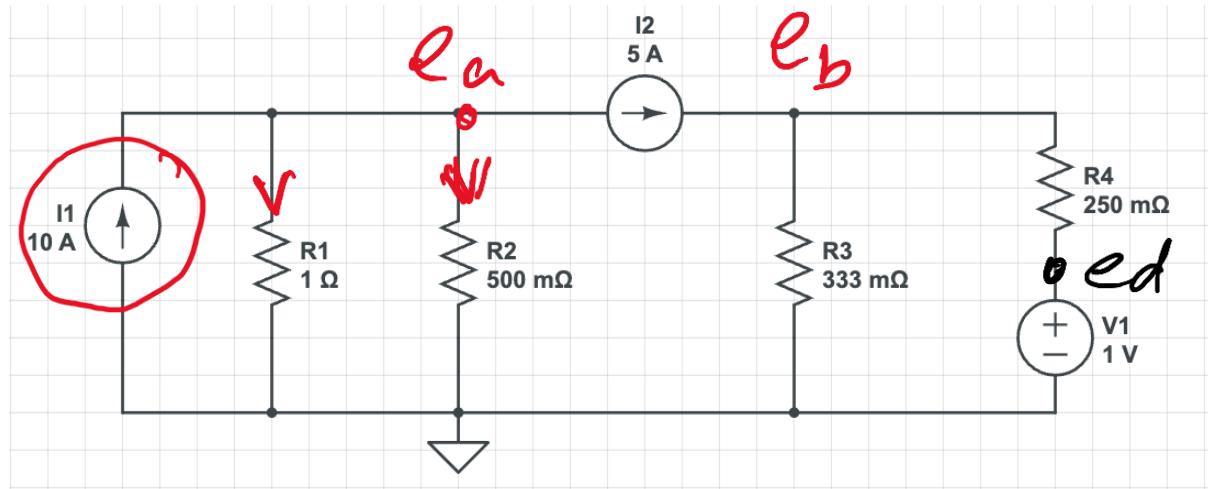


$$e_a \left(\frac{1}{1} + \frac{1}{0.5} \right) + 5 - 10 = 0$$

$$e_b \left(\frac{1}{0.333} + \frac{1}{0.25} \right) - \frac{1}{0.25} = 5$$

$$e_a = 1.67 \text{ V}$$

$$e_b = 1.288 = \frac{9}{7}$$

Example 5

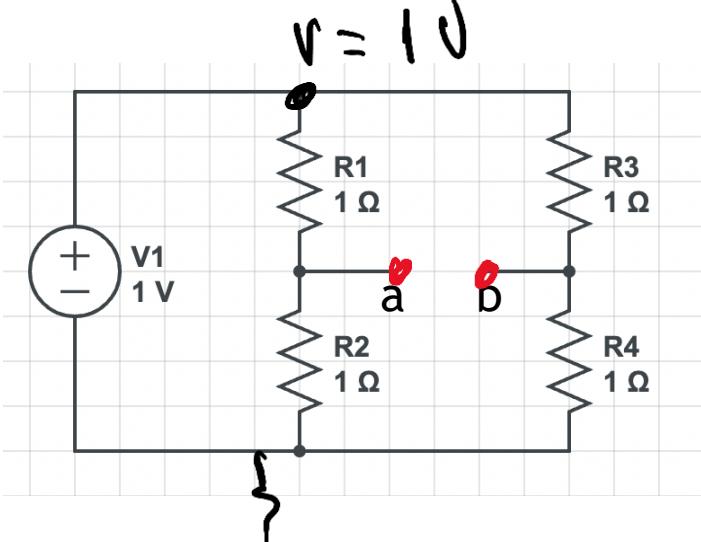


Find Thevenin's and Norton's at
a - b .

$$V_a \quad \text{and} \quad V_b$$



$$V_a = \frac{1}{2} \cdot 1 = 0.5V$$

$$V_b = 0.5V$$

$$\underline{V_{ab} = 0}$$

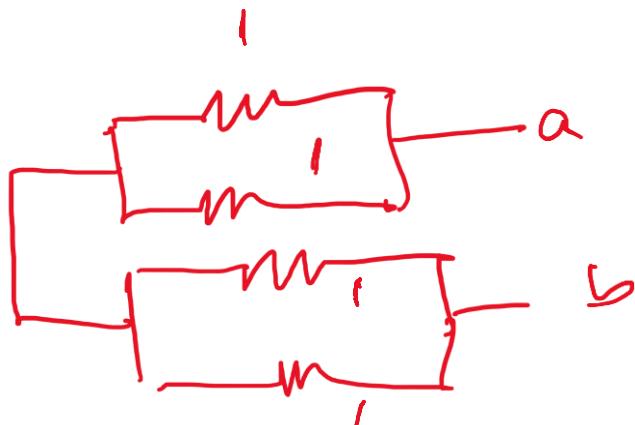

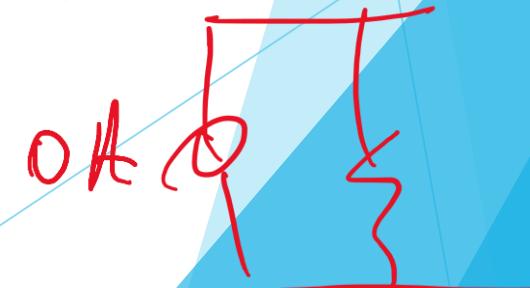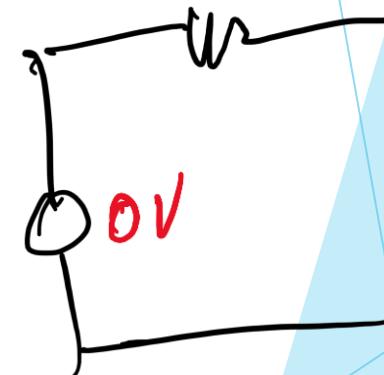
$$\begin{aligned} V_{ab} &= V_a - V_b \\ V_a &= \frac{1}{2} \cdot R_2 \\ &= \frac{1}{2 \cdot (R_1 + R_2)} \cdot V_s \\ &= 0.5V \end{aligned}$$



$$m^2 + m + \text{constant} = 0$$

Example 6

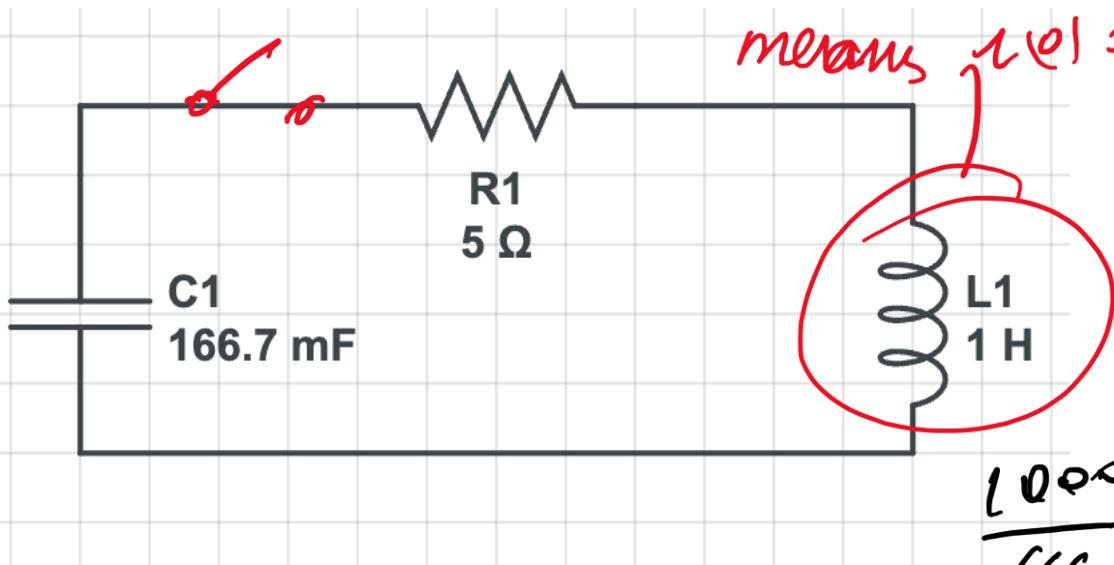

Series inductor means $i(0) = 0$

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = 0$$

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

$$\frac{1}{C} = \frac{1}{166.7 \times 10^{-3}} = 6$$

$$\frac{1}{C}$$

$$m^2 + 5m + 6 = 0 = \frac{1}{166.7 \times 10^{-3}}$$

$$(m+2)(m+3) = 0$$

$$\frac{1}{166.7 \times 10^{-3}}$$

$$m = -2 ; m = -3$$

$$i(t) = A_1 e^{-2t} + A_2 e^{-3t}$$

The initial current in the inductor is 0 amp. The initial voltage on the capacitor is $10V$. Find $i(t)$ in the circuit below.

$$v(0) = ? = 0 \quad A_1 + A_2 = 0$$

$$L \frac{di(0)}{dt} = -\frac{1}{C} \int v dt$$


v_0
Voltage
on C

$$\frac{di}{dt}(0) = -\frac{v_0}{L} = 10$$

$$A_1 + A_2 = 0$$

$$-2A_1 - 3A_2 = 10$$


Example 7

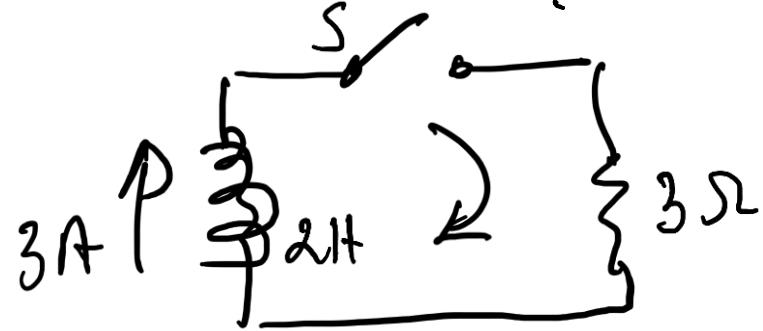

S closed at $t=0$

$$i(t) = 3 e^{-\frac{3}{2}t}$$

$$\frac{L di}{dt} + R i = 0$$

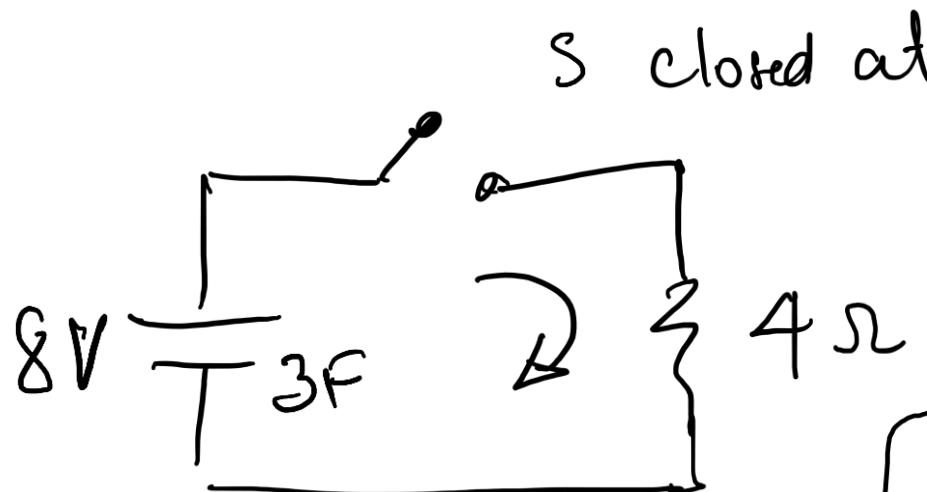

$$\frac{1}{RC} = \frac{1}{3.4} = \frac{1}{12}$$

$\frac{V}{R} = I_0$

S closed at $t=0$

$$R i + \frac{1}{C} \int i dt = 0$$

$$i(t) = 2 e^{-\frac{1}{12}t}$$

$$A e^{-\frac{1}{12}t}$$

$$L \frac{di}{dt} + Ri + \frac{1}{e} \int i dt = 0$$

$$m^2 + 4m + 4 = 0$$

$$(m+2)(m+2) = 0$$

$m = -2$ twice

$$i(t) = \underline{A_1 e^{-2t}} + A_2 \underline{t e^{-2t}}$$

rule for def. eqn.