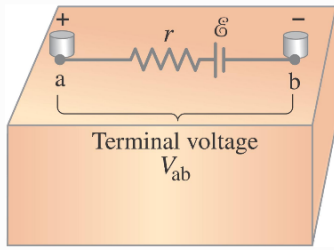


Chapter 26: DC Circuits


Emf and Terminal Voltage:



$$V_{ab} = \mathcal{E} - Ir \rightarrow \text{internal resistance of battery}$$

\hookrightarrow EMF

Example 26.1

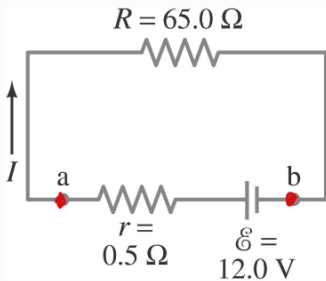

a) $V_{ab} = \mathcal{E} - Ir$, Ohm's law: $V_{ab} = IR$


$$IR = \mathcal{E} - Ir \Rightarrow I = \mathcal{E} / (R + r)$$

$$I = \frac{12.0 \text{ V}}{(65 + 0.5) \Omega} \Rightarrow I = 0.183 \text{ A}$$

b) $V_{ab} = \mathcal{E} - Ir = 12.0 \text{ V} - (0.183 \text{ A})(0.5 \Omega) \Rightarrow V_{ab} = 11.9 \text{ V}$

c) $P = I^2 R$, $P_R = (0.183 \text{ A})^2 (65.0 \Omega) = 2.16 \text{ W}$, $P_r = (0.183 \text{ A})^2 (0.5 \Omega) = 0.02 \text{ W}$

Resistors in Series configuration:

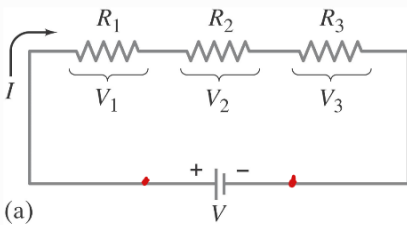


$$V = V_1 + V_2 + V_3, \quad V = IR_{eq}$$

$$IR_{eq} = IR_1 + IR_2 + IR_3 = I(R_1 + R_2 + R_3)$$

$$R_{eq} = R_1 + R_2 + R_3$$


Resistors in Parallel configuration:

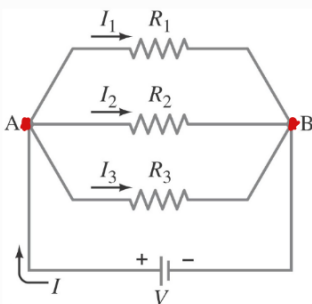

$$I = I_1 + I_2 + I_3, \quad I = \frac{V}{R_{eq}}$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Example 26.4

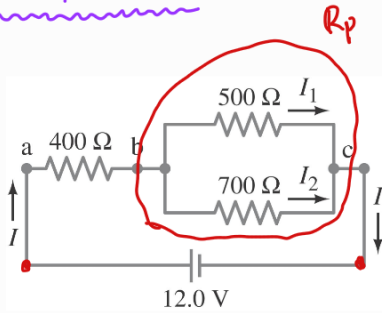


$$\frac{1}{R_p} = \frac{1}{500 \Omega} + \frac{1}{700 \Omega} = 0.0020 \Omega^{-1} + 0.0014 \Omega^{-1} = 0.0034 \Omega^{-1}$$

$$R_p = 1 / 0.0034 \Omega^{-1} \Rightarrow R_p = 290 \Omega$$

$$R_{eq} = R_p + 400 \Omega \Rightarrow R_{eq} = 290 \Omega + 400 \Omega = 690 \Omega, \quad V = I R_{eq}$$

$$I = V / R_{eq} = 12.0 \text{ V} / 690 \Omega = 0.0174 \text{ A} \approx 17 \text{ mA}$$

Example 26.5

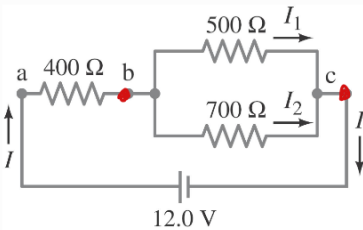

$$V_{ac} = V_{ab} + V_{bc}, \quad V_{ab} = (0.0174 \text{ A})(400 \Omega) = 7.0 \text{ V}$$

$$V_{bc} = 12.0 \text{ V} - 7.0 \text{ V} = 5.0 \text{ V}$$

$$I_1 = (5.0 \text{ V}) / (500 \Omega) = 1.0 \times 10^{-2} \text{ A} = 10 \text{ mA}$$

$$I_2 = (5.0 \text{ V}) / (700 \Omega) = 7 \text{ mA}$$

$$\left. \begin{array}{l} I_1 = 10 \text{ mA} \\ I_2 = 7 \text{ mA} \end{array} \right\} I_1 + I_2 = I$$