

Chapter 25: Electric Currents and Resistance

Electric Current:

$$\bar{I} = \frac{\Delta Q}{\Delta t}, \text{ instantaneous current: } I = \frac{dQ}{dt}. \text{ In SI units, } 1\text{A} = 1\text{C/s}.$$

Example 25.1


$$I = 2.5\text{A}$$

$$\Delta t = 4.0\text{min}$$

$$a) \Delta Q = I \Delta t = (2.5\text{A})(240\text{s}) \Rightarrow Q = 600\text{C}$$

$$b) 600\text{C} / (1.6 \times 10^{-19}\text{C}) = 3.8 \times 10^{21} \text{ electrons}$$


Ohm's Law:

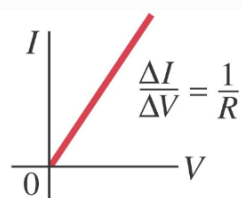

rate of voltage to current is resistance: $I = \frac{V}{R}$, $V = IR$.

→ an ohmic material

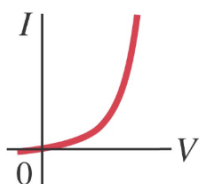In SI, the unit of R : $1\Omega = 1\text{V/A}$.



→ non-ohmic material

Example 25.4

$$a) I = 300\text{mA} = 0.3\text{A}, V = 1.5\text{V} \Rightarrow R = V/I = (1.5/0.3)\Omega = 5.0\Omega$$


$$b) V = 1.2\text{V}, R = 5.0\Omega \Rightarrow I = V/R = (1.2/5.0)\text{A} = 0.24\text{A}$$

Resistivity:

$$R = \rho \frac{L}{A}$$

ρ → resistivity
 L → length of the wire
 A → cross-sectional area

Example 25.5

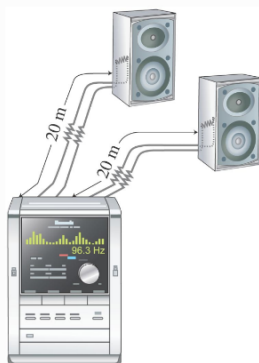

$$a) A = \rho \frac{L}{R}$$

$$A = (1.68 \times 10^{-8}) \frac{20\text{m}}{0.10\Omega} = 3.4 \times 10^{-6}\text{m}^2$$

$$\pi r^2 = A \Rightarrow r = 1.04 \times 10^{-3}\text{m}$$

$$d = 2r = 2.08 \times 10^{-3}\text{m}$$

$$b) V = IR$$

$$V = (4.0\text{A})(0.10\Omega) = 0.40\text{V}$$

Temperature dependence of Resistivity:

$$\rho_T = \rho_0 [1 + \alpha(T - T_0)]$$

ρ_0 $\rightarrow$ resistivity at T_0
 ρ_T $\rightarrow$ resistivity at T

$\alpha \rightarrow$ Temperature coefficient ($1/^\circ\text{C}$)

Example 25.7

$$T_0 = 20.0^\circ\text{C}$$

$$R_0 = 164.2 \Omega$$

$$R = 187.4 \Omega$$

$$T = ?$$

$$R = R_0 [1 + \alpha(T - T_0)] \quad , \quad \alpha = 3.927 \times 10^{-3} (^\circ\text{C}^{-1})$$

$$T = T_0 + \frac{R - R_0}{\alpha R_0} = 20^\circ\text{C} + \frac{187.4 \Omega - 164.2 \Omega}{(3.927 \times 10^{-3} ^\circ\text{C}^{-1})(164.2 \Omega)} = 56.0^\circ\text{C}$$

Electric Power

$$P = \frac{dU}{dt}, \quad U = qV \Rightarrow P = \frac{d(qV)}{dt} \Rightarrow P = \frac{dq}{dt} V = IV$$

Recalling Ohm's law: $P = IV = I^2 R = V^2 / R$

Example 25.8

$$P = V^2 / R \Rightarrow R = V^2 / P \Rightarrow R = (12\text{V})^2 / 40\text{W} = 3.6 \Omega$$



Alternating Current:

Voltage varies sinusoidally in time:

$$V = V_0 \sin(2\pi f t), \quad 2\pi f = \omega \Rightarrow V = V_0 \sin \omega t$$

$$I = V/R = \underbrace{(V_0/R)}_{I_0} \sin \omega t = I_0 \sin \omega t$$

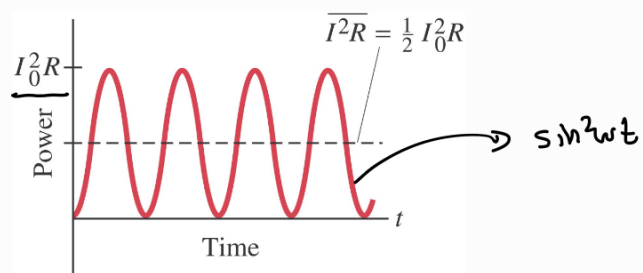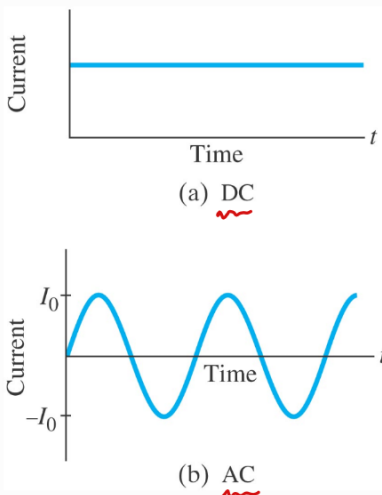Power is given by $P = I^2 R = I_0^2 R \sin^2 \omega t$



Average Power: $\bar{P} = I_0^2 R \overline{\sin^2 \omega t} \Rightarrow \bar{P} = \frac{1}{2} I_0^2 R = \frac{1}{2} \frac{V_0^2}{R}$

* The current and voltage have vanishing averages, thus we define RMS values:

$$I_{rms} = \sqrt{\overline{I^2}} = \frac{I_0}{\sqrt{2}} = 0.707 I_0, \quad V_{rms} = \sqrt{\overline{V^2}} = \frac{V_0}{\sqrt{2}} = 0.707 V_0$$

Example 25.13

$$\bar{P} = 1000 \text{ W}$$

$$V_{rms} = 120 \text{ V}$$

a) $I_0 = ? \Rightarrow I_0 = \sqrt{2} I_{rms} = \sqrt{2} (8.33 \text{ A}) = 11.8 \text{ A}$

$$\bar{P} = I_{rms} V_{rms} \Rightarrow I_{rms} = \bar{P} / V_{rms} = 1000 / 120 \text{ A} = 8.33 \text{ A}$$

$$R = V_{rms} / I_{rms} \Rightarrow R = 120 \text{ V} / 8.33 \text{ A} = 14.4 \Omega$$