

May 10, 2022

EEE 208 ELECTRIC CIRCUIT ANALYSIS II
EEE 202 ELECTRIC CIRCUITS II

SPRING'22 - MIDTERM EXAM

SOLUTIONS

Name: _____, Signature: _____

Closed books and closed notes. Use of mobile phones is considered cheating. Show your work clearly in the spaces provided. Otherwise, no credit will be given.

- (22 pts) Q.1 The input to the circuit shown in the following figure is the source voltage $v_s(t)$. The output is the resistor voltage $v_o(t)$. Determine the output voltage when the circuit is at steady state and the input is $v_s(t) = 25 \cos(100t - 15^\circ)$ V.

Using phasor method,
we get

$$\bar{V}_s(\omega) = 25 \angle -15^\circ \text{ V}$$

$$\bar{Z}_L = j\omega L = j100 \times 5 = j500 \Omega$$

$$\bar{Z}_C = \frac{-j}{\omega C} = \frac{-j}{100 \times 2 \times 10^{-3}} = -j5 \Omega$$



Applying KVL to the
supermesh, we obtain

$$j500\bar{I}(\omega) - j5 \times 10\bar{I}(\omega) + 40 \times 10\bar{I}(\omega) = 25 \angle -15^\circ$$

$$\begin{aligned} \text{Thus, } \bar{I}(\omega) &= \frac{25 \angle -15^\circ}{400 + j450} = \frac{25 \angle -15^\circ}{602 \angle 48.37^\circ} \\ &= 0.004152 \angle -63.37^\circ \text{ A} \end{aligned}$$


$$\bar{V}_o(\omega) = 40 \times 10\bar{I}(\omega) = 16.61 \angle -63.37^\circ \text{ V}$$
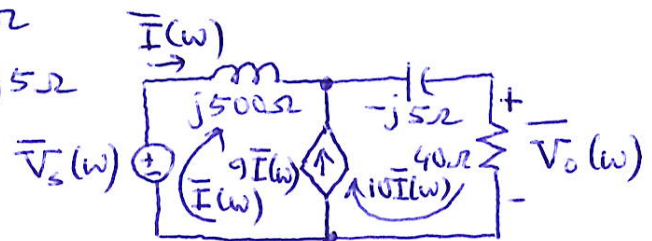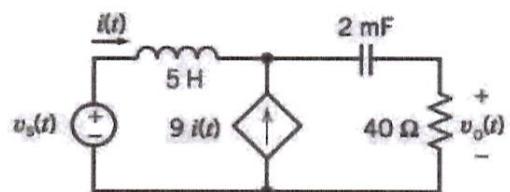
$$\text{Therefore, } v_o(t) = 16.61 \cos(100t - 63.37^\circ) \text{ V}$$



The circuit in the
frequency domain

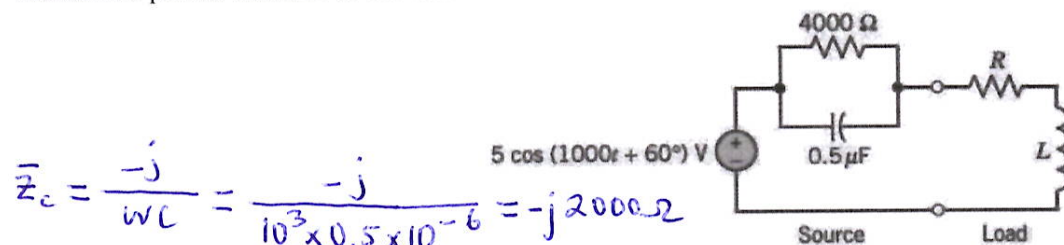- (22 pts) Q.2 Determine values of R and L for the circuit shown in the following figure that cause maximum power transfer to the load.



$$\bar{Z}_c = \frac{-j}{\omega C} = \frac{-j}{10^3 \times 0.5 \times 10^{-6}} = -j2000 \Omega$$

$$\begin{aligned} \bar{Z}_t &= (4000 \parallel -j2000) \Omega \\ &= \frac{4000(-j2000)}{4000 - j2000} = 800 - j1600 \Omega \end{aligned}$$

$$\bar{Z}_L = \bar{Z}_t^* = 800 + j1600 \Omega$$

Therefore,

$$\bar{Z}_L = R + j1000 L = 800 + j1600$$

$$R = 800 \Omega \quad \text{and} \quad L = \frac{1600}{1000} = 1.6 \text{ H}$$


- (20 pts) Q.3 Determine the complex power delivered to the three-phase load of a three-wire Y-to-Y circuit such as the one shown in the following figure. The phase voltages of the Y-connected source are $V_a = 110 \angle 0^\circ$ V rms, $V_b = 110 \angle -120^\circ$ V rms, and $V_c = 110 \angle 120^\circ$ V rms. The load impedances are $Z_A = Z_B = Z_C = 50 + j80 \Omega$.

The complex power delivered to the three-phase load is three times the complex power delivered to the single-phase load if the circuit is a balanced three-phase circuit. As given, load

impedances are equal; phase voltages have identical amplitude and are out of phase with each other by 120° . Thus, the given circuit is a balanced three-phase one. Then,

$$\bar{I}_{aA} = \frac{\bar{V}_a}{\bar{Z}_A} = \frac{110 \angle 0^\circ}{50 + j80} = \frac{110 \angle 0^\circ}{94.34 \angle 58^\circ} = 1.16 \angle -58^\circ \text{ A rms}$$
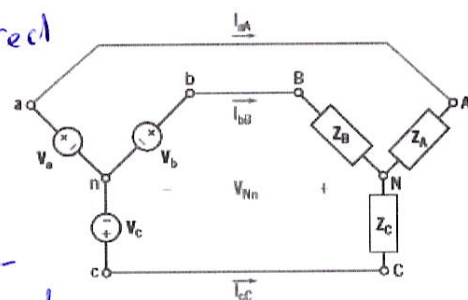
$$\begin{aligned} \text{The complex power delivered to the three-phase load is} \\ 3 \bar{S}_A &= 3 \bar{V}_a \bar{I}_{aA}^* = 3 (110 \angle 0^\circ) (1.16 \angle -58^\circ)^* \\ &= 3 \times 110 \times 1.16 \angle 58^\circ = 382.80 \angle 58^\circ = 203 + j325 \text{ VA} \end{aligned}$$



- (20 pts) **Q.4** Two electrical loads are connected in parallel to a 400-V rms, 50-Hz supply. The first load is 12 kVA at 0.7 lagging power factor; the second load is 10 kVA at 0.8 lagging power factor. Find the average power, the apparent power, and the power factor of the two combined loads.

$$\text{Load 1: } P_1 = |\bar{S}| \cos \theta = (12 \text{ kVA}) (0.7) = 8.4 \text{ kW}$$

$$Q_1 = |\bar{S}| \sin(\cos^{-1} 0.7) = (12 \text{ kVA}) \sin 45.6^\circ \\ = 8.57 \text{ kVAR}$$

$$\text{Load 2: } P_2 = (10 \text{ kVA}) (0.8) = 8 \text{ kW}$$

$$Q_2 = (10 \text{ kVA}) \sin(\cos^{-1} 0.8) = 10 \sin 36.9^\circ \\ = 6 \text{ kVAR}$$

$$\text{Total: } \bar{S} = P + jQ = (8.4 + 8) + j(8.57 + 6) \\ = 16.4 + j14.57 = 21.9 \angle 41.6^\circ \text{ kVA}$$


The average power is $P = 16.4 \text{ kW}$

The apparent power is $S = |\bar{S}| = \sqrt{P^2 + Q^2} = 21.9 \text{ kVA}$

The power factor is $\text{pf} = \cos 41.6^\circ = 0.75 \text{ lagging}$.

- (16 pts) **Q.5** Find the rms value of the current waveform shown in the following figure.
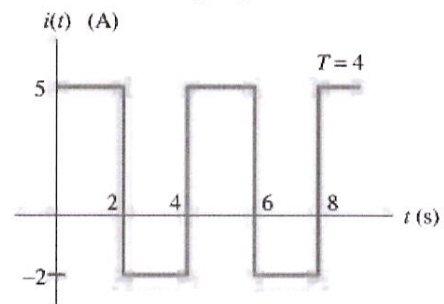
$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}, \quad T = 4 \text{ s} \\ = \sqrt{\frac{1}{4} [5^2 \times 2 + (-2)^2 \times 2]} \\ = \sqrt{\frac{1}{4} (50 + 8)} \\ = \sqrt{\frac{58}{4}} \\ = 3.808 \text{ A.}$$



Useful Info:

Phasors:

$$\begin{aligned} \mathbf{V}(\omega) &= V_m e^{j\theta_v} = V_m \angle \theta_v & \mathbf{I}(\omega) &= I_m e^{j\theta_i} = I_m \angle \theta_i & e^{\pm j\theta} &= \cos \theta \pm j \sin \theta \\ \mathbf{V}_L(\omega) &= Z_L \mathbf{I}_L(\omega) & \mathbf{V}_C(\omega) &= Z_C \mathbf{I}_C(\omega) & \mathbf{V}_R(\omega) &= Z_R \mathbf{I}_R(\omega) \\ Z_L &= j\omega L & Z_C &= 1/j\omega C & Z_R &= R \end{aligned}$$

Note that ω is the angular frequency, which is $2\pi f$.

The **rms** value of a periodic waveform $w(t)$ is defined as: $W_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} w^2(t) dt}$

For a **sinusoidal waveform** $v(t) = V_m \cos(\omega t + \theta)$: $V_{rms} = \frac{V_m}{\sqrt{2}}$

Equivalent impedance when the impedances are in series $Z_{eq} = \sum_{i=1}^k Z_i = Z_1 + Z_2 + \dots + Z_k$.

Equivalent impedance when the impedances are in parallel $\frac{1}{Z_{eq}} = \sum_{i=1}^k \frac{1}{Z_i} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_k}$.

The **average power** $P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$. The **reactive power** $Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$.

The **complex power** $\mathbf{S} = \frac{\mathbf{V}\mathbf{I}^*}{2} = \frac{V_m I_m}{2} \angle(\theta_v - \theta_i) = V_{rms} I_{rms} \angle(\theta_v - \theta_i) = P + jQ$.

The **apparent power** is $|\mathbf{S}| = \frac{V_m I_m}{2}$. The **power factor** $pf = \cos(\theta_v - \theta_i)$.

For the **maximum power transfer**, $Z_L = Z_t^*$, where Z_L is the load impedance and Z_t^* is the complex conjugate of the Thévenin equivalent impedance Z_t of the circuit.

For **coupled inductors** in the time domain $v_1 = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt}$ and $v_2 = L_2 \frac{di_2}{dt} \pm M \frac{di_1}{dt}$

For an **ideal transformer**, $\mathbf{V}_2 = \frac{N_2}{N_1} \mathbf{V}_1$ and $\mathbf{I}_1 = -\frac{N_2}{N_1} \mathbf{I}_2$.

Total complex power in a **balanced three-phase** circuits: $\mathbf{S}_T = 3\mathbf{S}_p = 3 \frac{\mathbf{V}\mathbf{I}^*}{2}$.

In **balanced three-phase** circuits, $V_{LL} = \sqrt{3}V_p$ and $I_L = I_p$ for Y connection; $V_{LL} = V_p$ and $I_L = \sqrt{3}I_p$ for Δ connection.

In an **ideal op-amp**: $i_+ = i_- = 0$ $v_+ = v_-$

Nano (**n**) $\rightarrow 10^{-9}$ Micro (**μ**) $\rightarrow 10^{-6}$ Milli (**m**) $\rightarrow 10^{-3}$ Kilo (**k**) $\rightarrow 10^3$ Mega (**M**) $\rightarrow 10^6$