

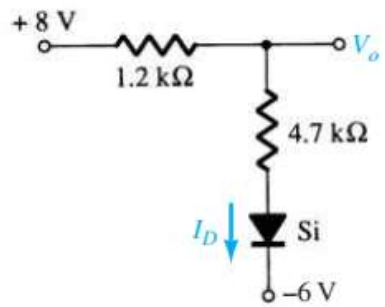


EEE206 Midterm Preparation



Example 1

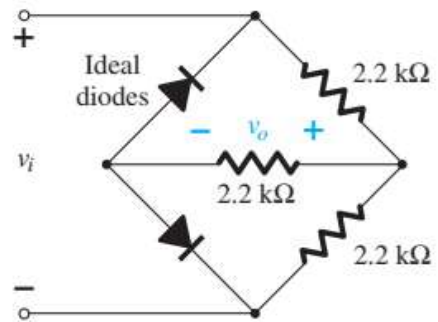


Example 2

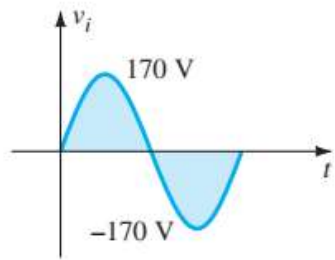

Example 3

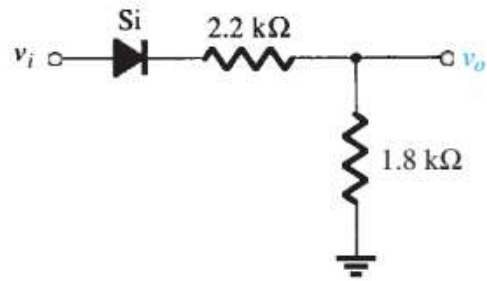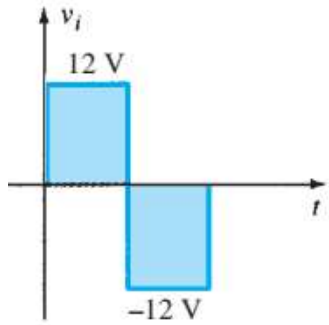

Example 4

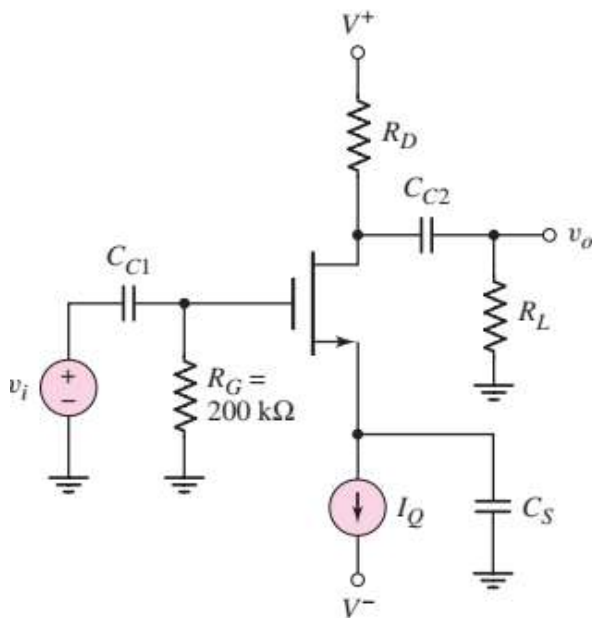


The transistor in the common-source amplifier in has parameters $V_{TN} = 0.8 \text{ V}$, $k_n = 2.50 \text{ mA/V}^2$, and $\lambda = 0.02 \text{ V}^{-1}$.

The circuit parameters are $V^+ = 5 \text{ V}$, $V^- = -5 \text{ V}$, $I_Q = 0.5 \text{ mA}$, and

$R_D = 6 \text{ k}\Omega$. (a) Determine V_{GSQ} and V_{DSQ} . (b) Find the small-signal voltage gain, R_o , R_i for $R_L = 20 \text{ k}\Omega$


Example 5

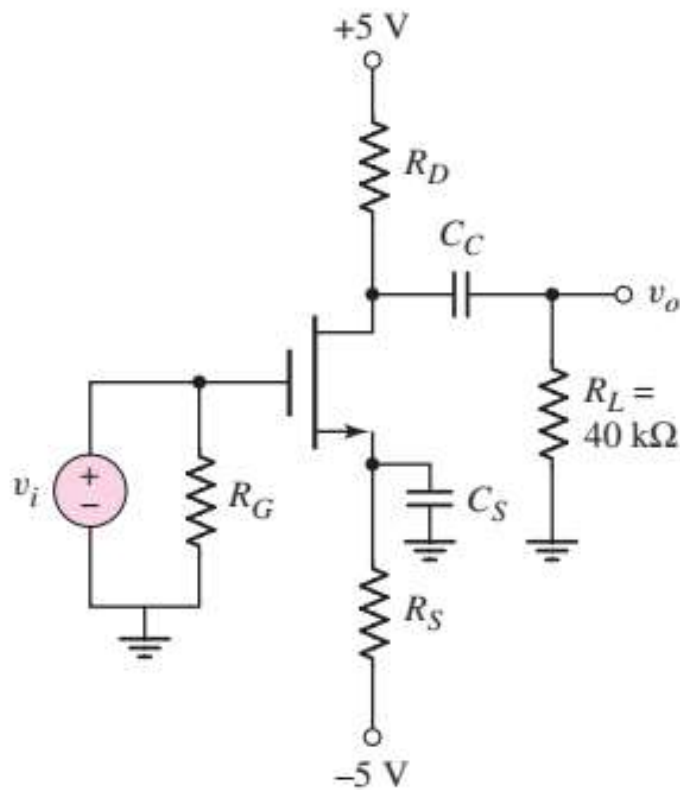

The parameters of the MOSFET in the circuit shown in Figure are $V_{TN} = 0.8\text{ V}$, $K_n = 0.85\text{ mA/V}^2$, and $\lambda = 0.02\text{ V}^{-1}$. (a) Determine R_S and R_D such that $I_{DQ} = 0.1\text{ mA}$ and $V_{DSQ} = 5.5\text{ V}$. (b) Find the small-signal transistor parameters. (c) Determine the small-signal voltage gain.

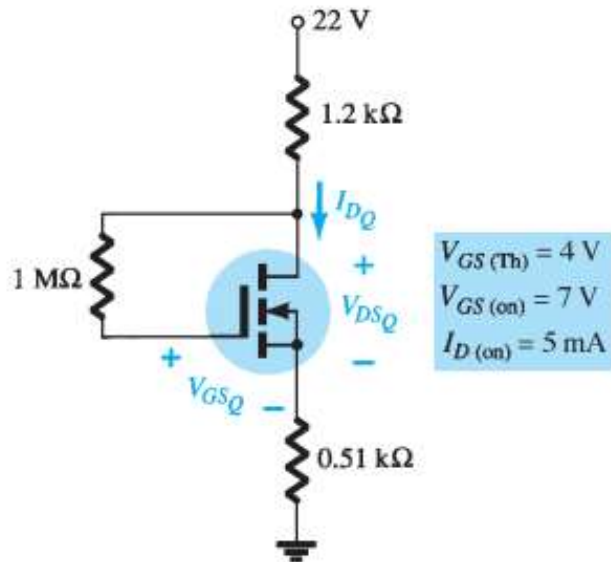Example 6


Find $V_G, V_S, V_D, V_{DSQ}, I_{DQ}$ and determine if we are in saturation or not



Enhanced mode NMOS


Example 7

Determine I_B , I_C , I_E , V_B , V_C , V_E . $\beta = 75$

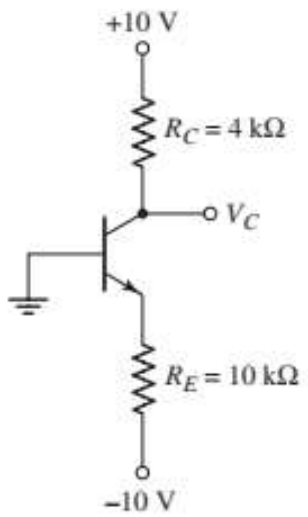

Example 8

$$\beta = 75.$$

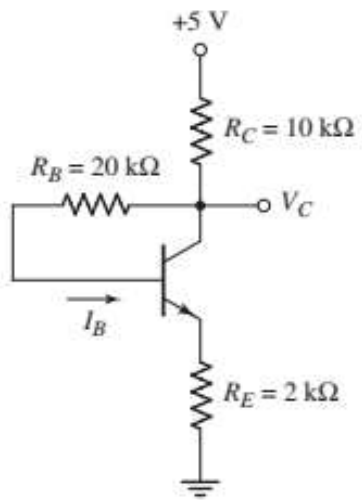

Example 9

